

$\omega = 1$, and the frequencies in those expressions are all scaled to the cut off frequency $\omega_c = 1$.

===== Series sections =====

The image impedances of the series section are given by

<formula>

and is the same as that of the constant k section

<formula>

===== Shunt sections =====

The image impedances of the shunt section are given by

<formula>

and is the same as that of the constant k section

<formula>

As with the k type section , the image impedance of the m type low pass section is purely real below the cut off frequency and purely imaginary above it . From the chart it can be seen that in the passband the closest impedance match to a constant pure resistance termination occurs at approximately $m = 0.6$.

===== Transmission parameters =====

For an m derived section in general the transmission parameters for a half section are given by

<formula>

and for n half sections

<formula>

For the particular example of the low pass L section , the transmission parameters solve differently in three frequency bands .

For <formula> the transmission is lossless :

<formula>

For <formula> the transmission parameters are

<formula>

For <formula> the transmission parameters are

<formula>

===== Prototype transformations =====